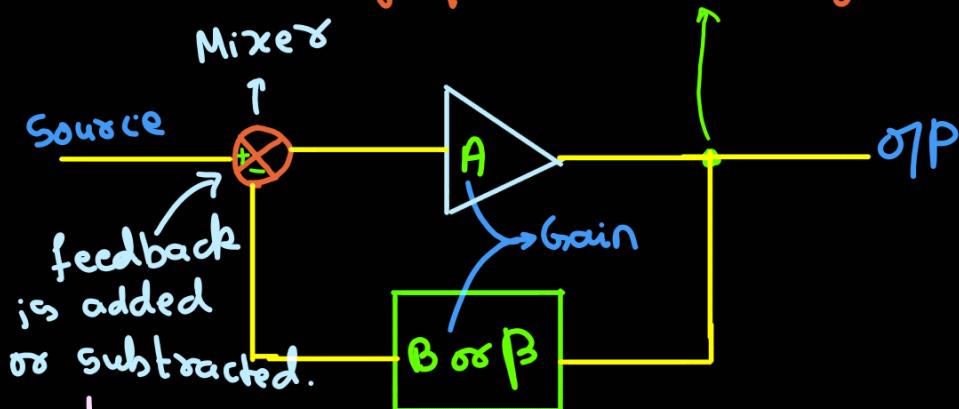



# Feedback Amplifiers
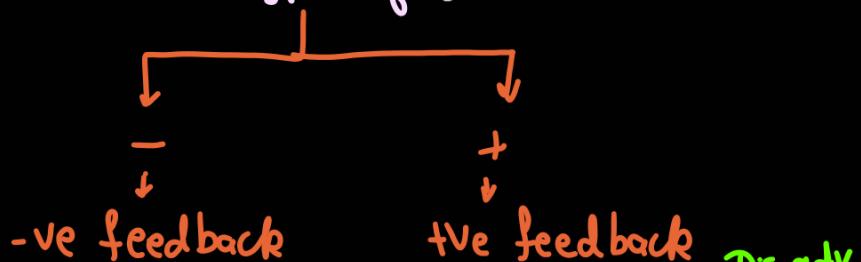
# Feedback :-

↳ Fraction of o/p is sampled & given back to i/p side.



↳ Based on this  $\rightarrow$  2 types of feedback.



# Why negative feedback?


Adv.

1. Desensitizes the Gain
2. Reduces a non-linear distortion.
3. Reduces the effect of noise
4. Modifies the i/p & o/p impedance
5. Increases bandwidth

All this is done at the cost of the reduction of overall gain

Disadv.
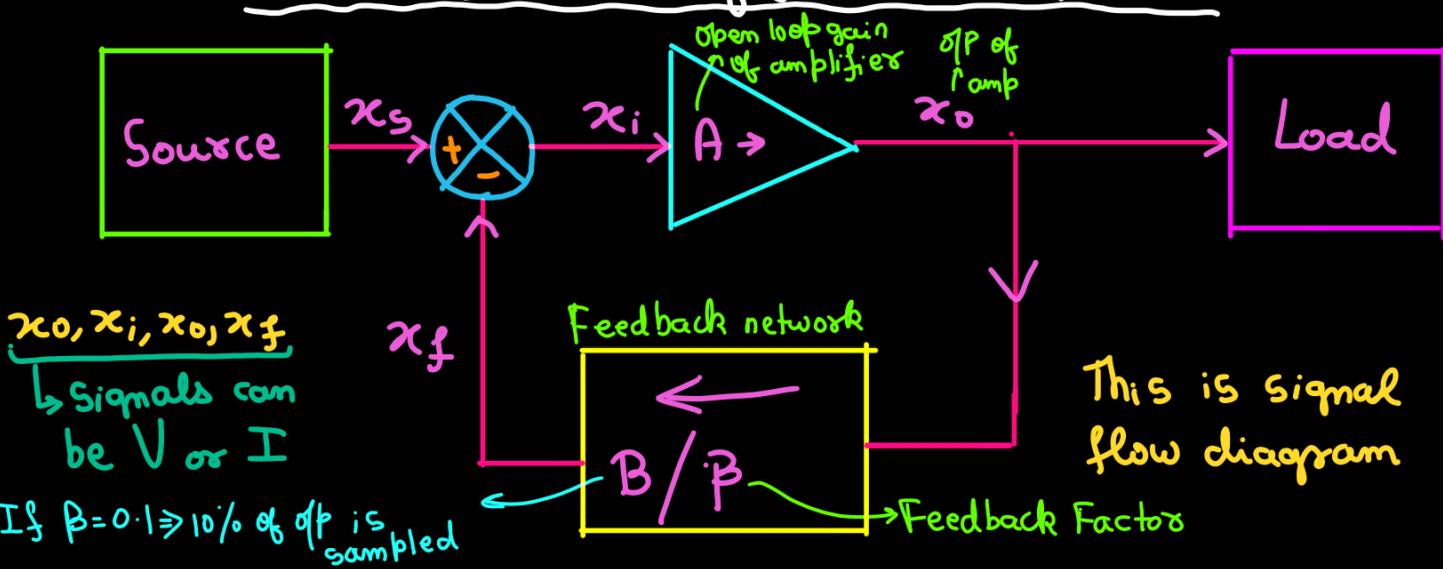
# General structure of feedback amplifiers:-



$$\left. \begin{array}{l} \text{Mathematically } \Rightarrow x_f = \beta x_o \\ x_o = A x_i \end{array} \right\} x_i = x_s - x_f$$

We want to find overall gain  $\Rightarrow \frac{x_o}{x_s}$

$$\frac{x_o}{A} = x_s - \beta x_o \Rightarrow \frac{x_o}{A} + \beta x_o = x_s \Rightarrow \frac{x_o}{x_s} = \frac{A}{1 + A\beta} = A_f$$

$A\beta \Rightarrow$  Loop Gain

↳ for -ve feedback

↳  $A\beta$  must be +ve


Gain of amplifier  
with feedback network.

Here,  $1 + A\beta = \text{Amount of feedback.}$

When  $A\beta \gg 1 \Rightarrow A_f = \frac{A}{A\beta} \approx \frac{1}{\beta}$   $\rightarrow$  Almost independent of the open loop gain  
↳ determined entirely by feedback network.

\* Easy to set precise value of the gain of the feedback amplifiers  $\Rightarrow$  made of passive elements

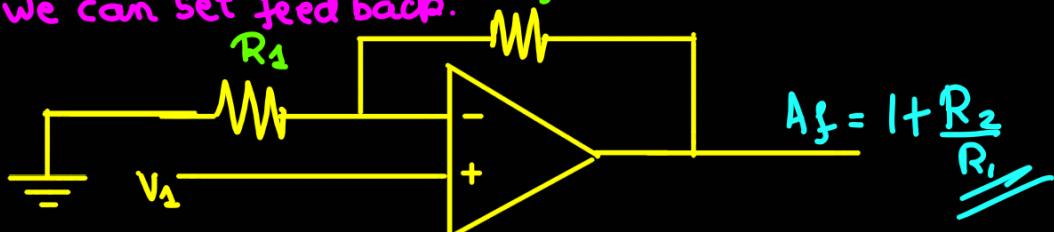Ex: Op-Amp has very high gain. Using simple resistors, we can set feedback.




$$\text{WKT, } x_o = \frac{A}{1 + A\beta} x_s \quad \left| \begin{array}{l} \text{WKT, } x_f = \beta x_o \\ \hline \end{array} \right.$$

$$\therefore x_f = \frac{A\beta}{1 + A\beta} x_s$$

If  $A\beta \gg 1 \Rightarrow x_f \approx x_s$

## #Feedback Topologies:-


Consider the general structure.

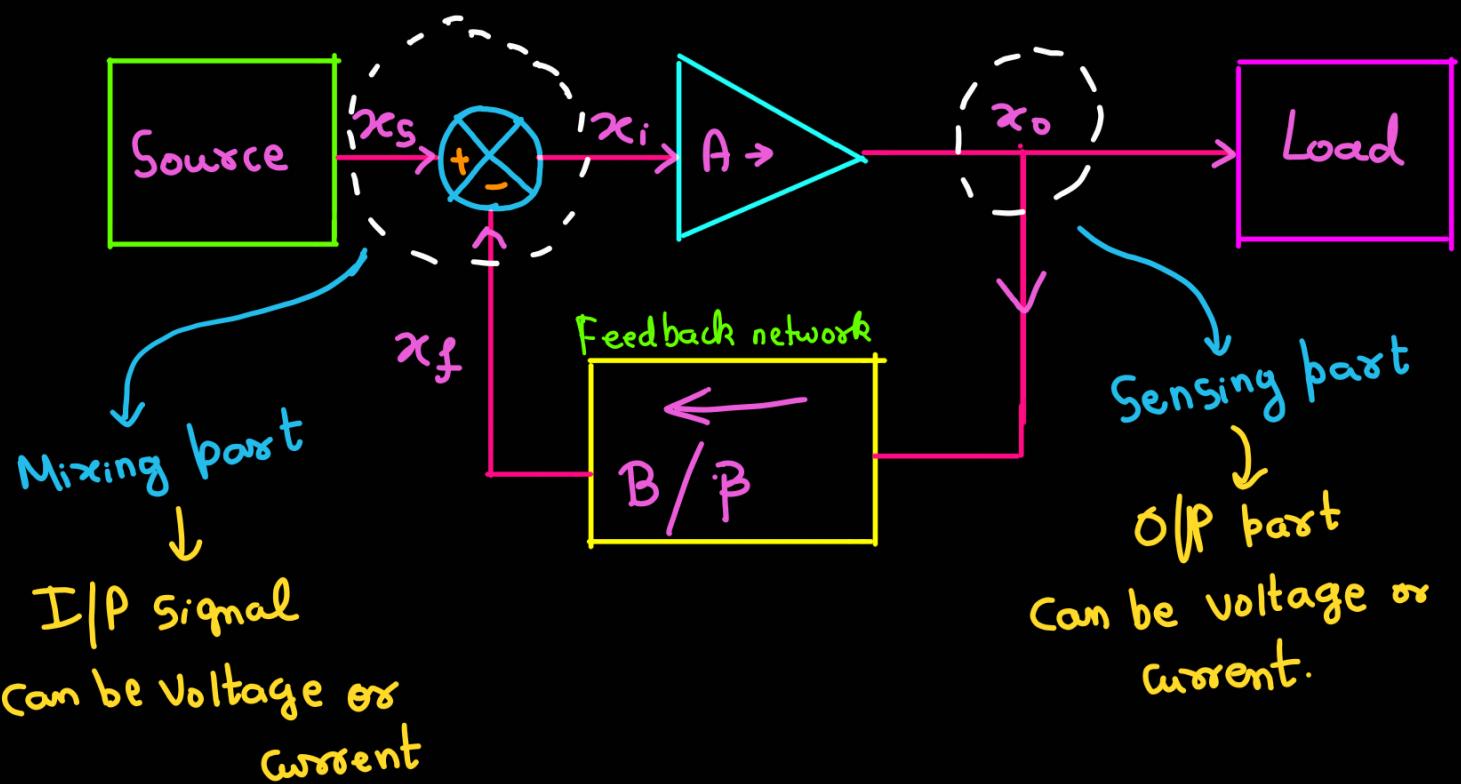

From the above, we have 4 topologies

1. Voltage Series Feedback
2. Voltage Shunt Feedback
- 3 Current Series Feedback
4. Current Shunt Feedback.

## #Voltage Series Feedback:-

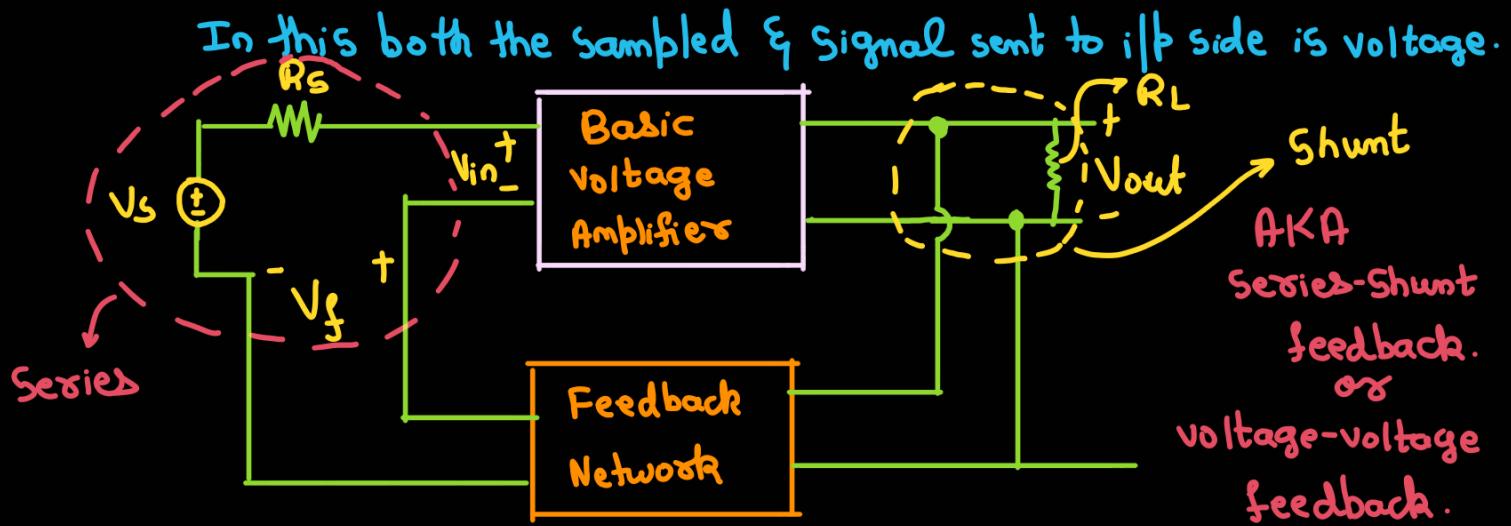

★ When we want to sample the voltage, then on o/p  $\Rightarrow$  shunt i/p or mixing  $\Rightarrow$  series


★ All voltage amplifiers use this topology

★ I/P & O/P impedances :-

→ Due to series connection i/p impedance will increase  
 $\hookrightarrow R_{if} = R_i(1 + A\beta)$

→ -V —||— shunt —||— O/p —||— decrease
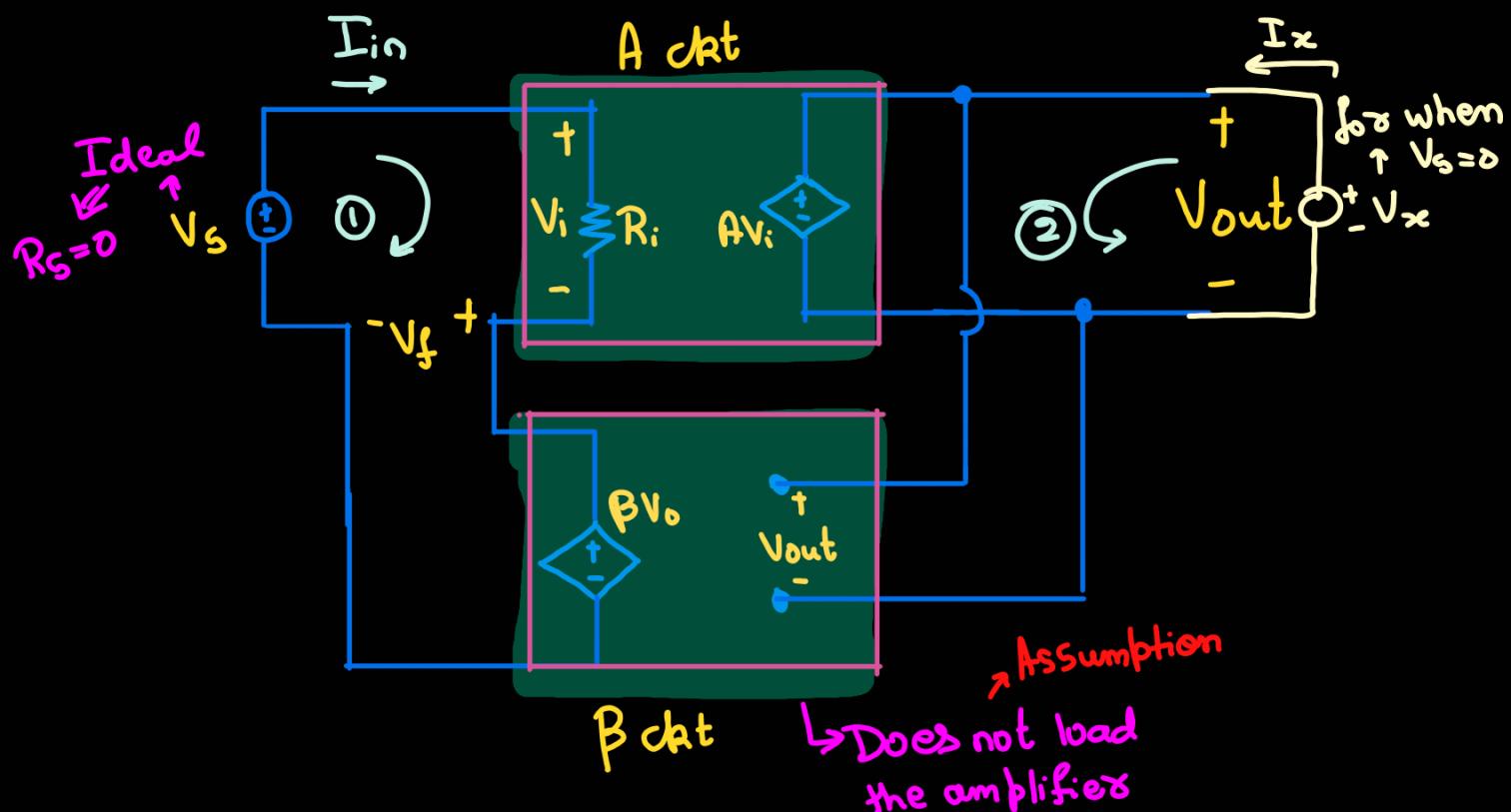
$$\hookrightarrow R_{of} = \frac{R_o}{1 + A\beta}$$



★ Effective I/P impedance :-

$$\text{As seen from source side } = R_{if} = \frac{V_s}{I_{in}}$$

$$\text{KVL in loop 1: } V_i = V_s - V_f = V_s - \beta V_o$$

$$I_{in} \times R_i = V_s - \beta V_o$$

$$\Rightarrow I_{in} R_i = V_s - A\beta V_{in}$$

$$\Rightarrow I_{in}R_i = V_s - A\beta [I_{in}X_{Ri}]$$

$$(1+A\beta)I_{in}X_{Ri} = V_s$$

$$\Rightarrow \frac{V_s}{I_{in}} = R_i(1+A\beta)$$

$$\Rightarrow R_{if} = R_i(1+A\beta)$$

i/p impedance increases

For o/p impedance  $\Rightarrow V_s = 0$  & apply test voltage to o/p side  
 ↳ Say  $V_x$

$$R_{of} = \frac{V_x}{I_x}$$

$$V_f = \beta V_x$$

Applying KVL in loop 1 but with  $V_s = 0$

$$\Rightarrow V_i = -V_f$$

Applying KVL in loop 2

$$\Rightarrow V_x = R_o I_x + A V_i$$

$$V_x = R_o I_x - A\beta V_x$$

$$V_x(1+A\beta) = R_o I_x$$


$$\frac{V_x}{I_x} = \frac{R_o}{(1+A\beta)} \Rightarrow R_{of} = \frac{R_o}{1+A\beta}$$

o/p impedance will reduce

This  $\uparrow$  in  $i/p$  impedance &  $\downarrow$  in  $o/p$  impedance is desired.

The actual / real amplifier ckt has  $R_s$  additionally.


Equivalent feedback ckt

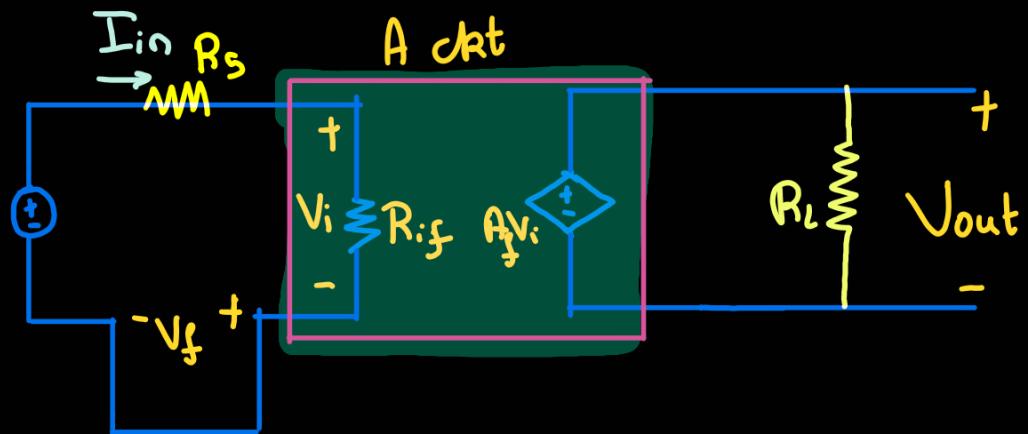


$$V_i = \frac{R_{if} \cdot V_s}{R_{if} + R_s}$$


$$V_{OL} = \frac{R_L}{R_{if} + R_L} \times A_f V_i$$

### # Voltage Shunt Feedback:-

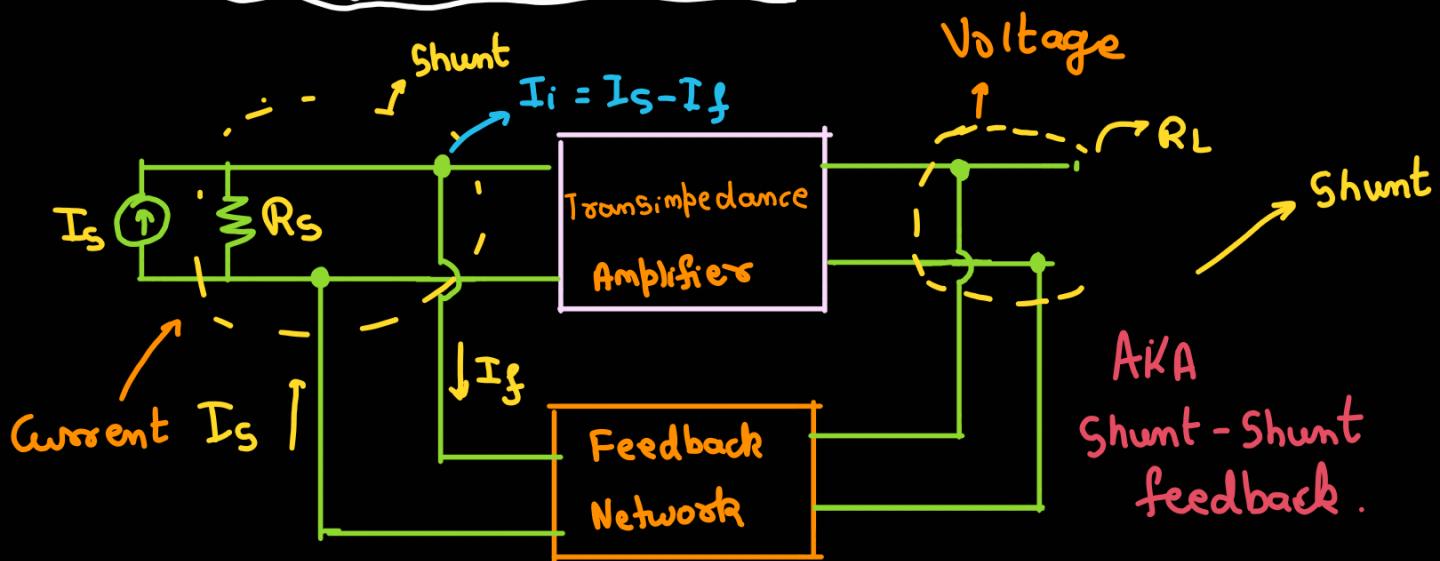

### Transimpedance Amplifier

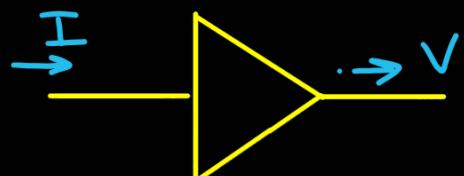

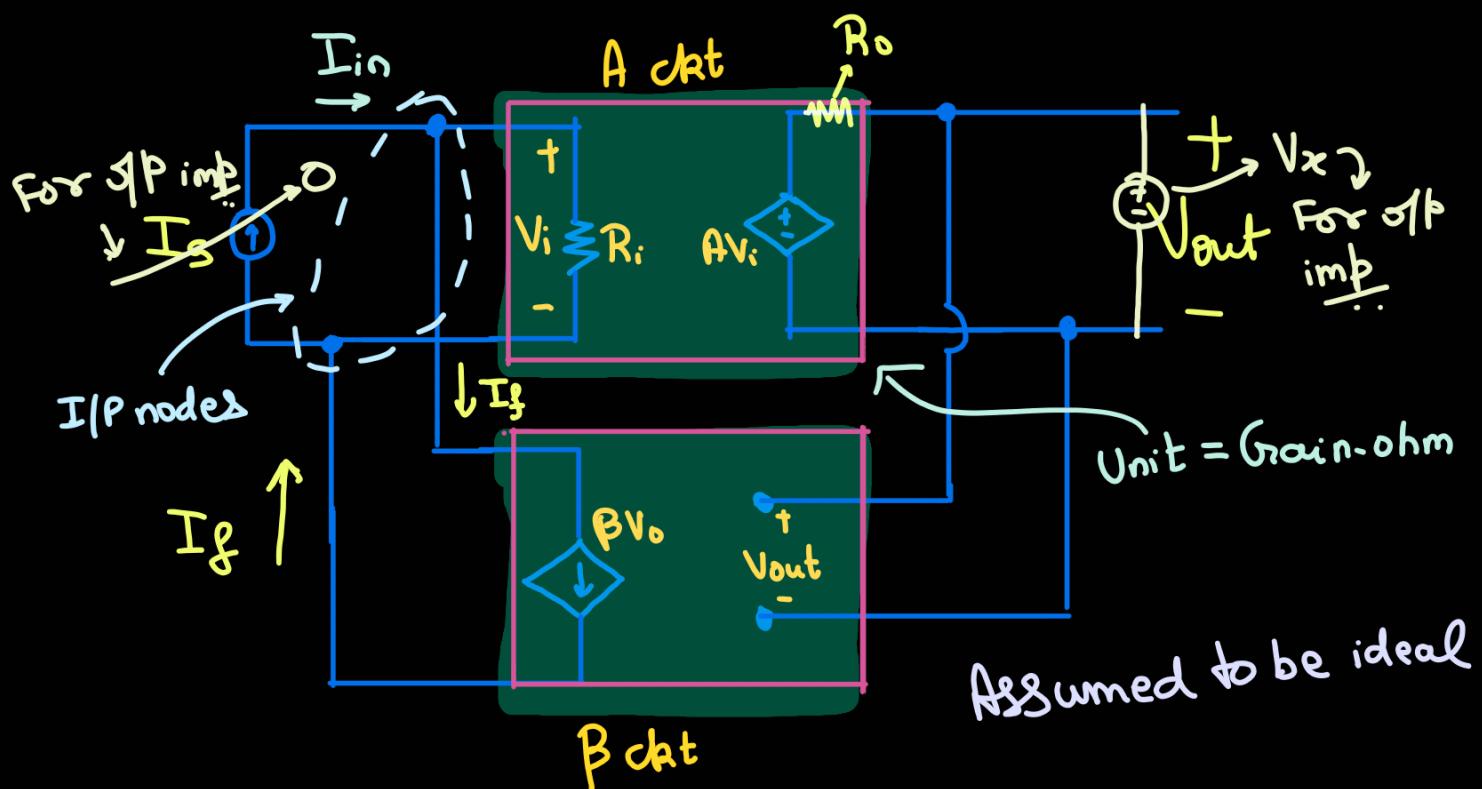

\* I/P & O/P impedances :-

Since both i/p & o/p ckt's are shunt, the i/p & o/p impedances will both reduce by a factor of  $1 + A\beta$

→ I/P impedance :-

$$R_{if} = \frac{V_i}{I_f} \quad | \text{ KCL to i/p node:-}$$

$$I_s - I_f = I_i$$

$$\Rightarrow I_s - \beta V_o = I_i$$

$$\Rightarrow I_s = I_i + \beta V_o = I_i + A\beta I_i$$

$$I_s = I_i(1 + A\beta)$$

$$I_s = \frac{V_i}{R_i} (1 + A\beta) \Rightarrow \frac{V_i}{I_s} = \frac{R_i}{1 + A\beta}$$

$\Rightarrow R_{if} = \frac{R_i}{1 + A\beta}$

\* O/P impedance :-


All independent sources are open circuited. Test voltage  $V_x$  applied on o/p side.

$$R_{of} = \frac{V_x}{I_x} \quad \left| \begin{array}{l} I_f = \beta V_x \\ \text{Applying KCL to i/p node.} \\ I_f = -I_i \Rightarrow \beta V_x = -I_i \end{array} \right.$$



WKT,

$$V_x = R_o I_x + A I_i$$
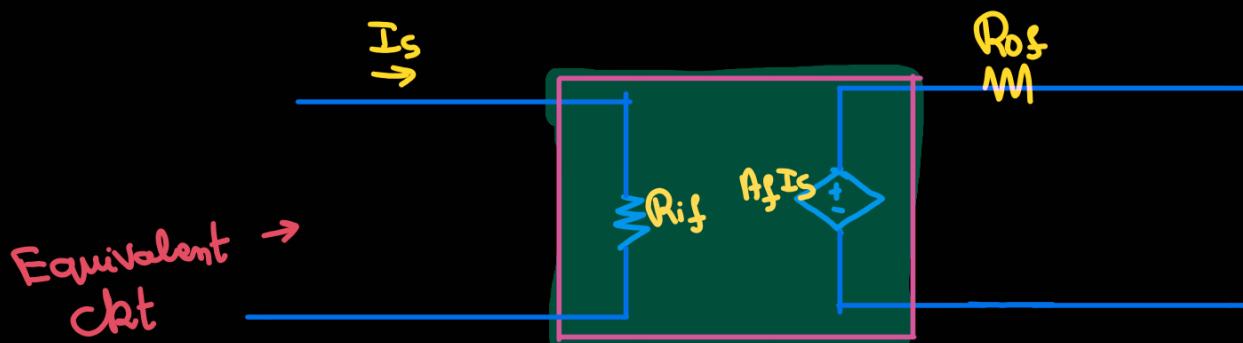
$$\begin{aligned} V_x &= R_o I_x - A\beta V_x \Rightarrow V_x [1 + A\beta] = R_o I_x \\ &\Rightarrow \frac{V_x}{I_x} = R_{of} = \frac{R_o}{1 + A\beta} \end{aligned}$$



## # Current Shunt Feedback :-

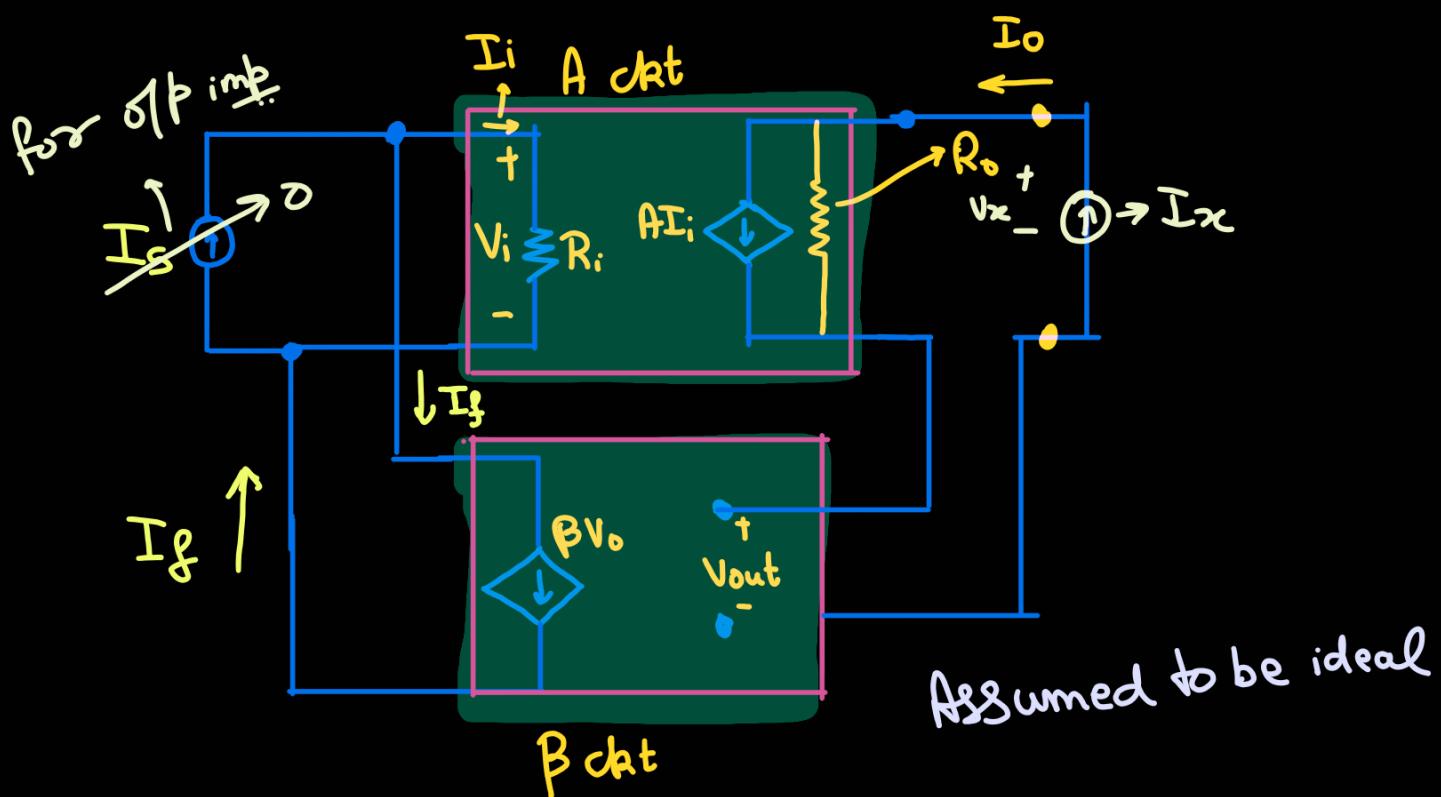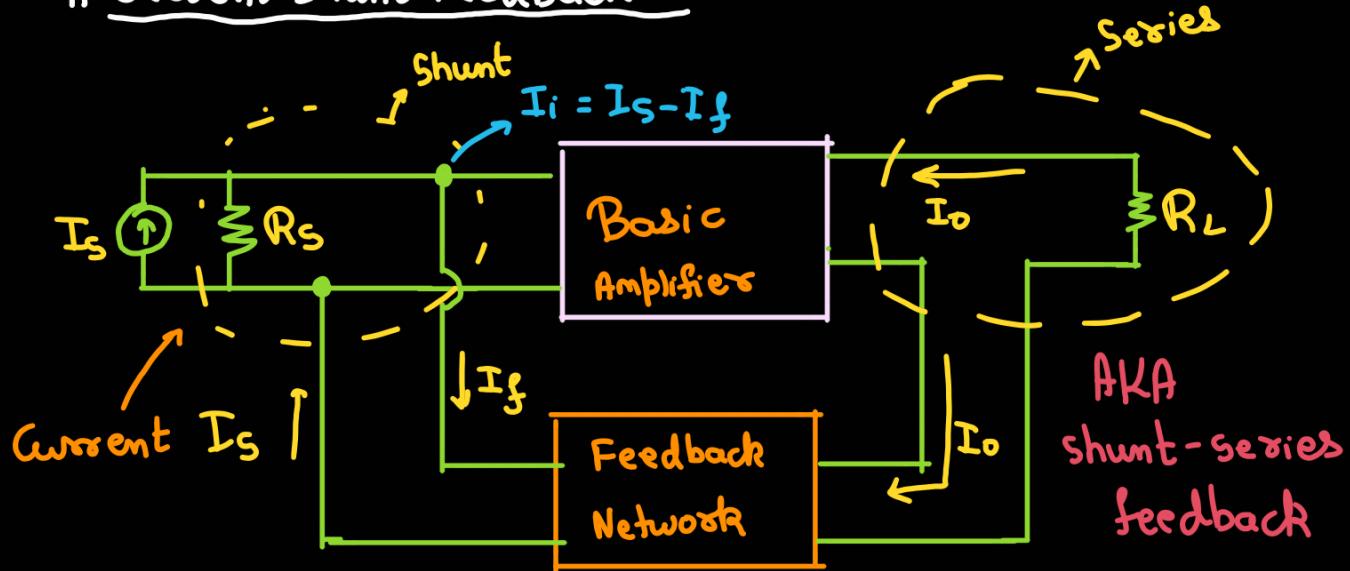

\* Effective i/p impedance

$$R_{if} = \frac{V_i}{I_f} \quad \left| \begin{array}{l} \text{Applying KCL to i/p nodes} \\ I_s - I_f = I_i \end{array} \right.$$

$$\Rightarrow I_s - \beta I_o = I_i \Rightarrow I_s - A\beta I_i = I_i$$

$$I_s = I_i (1 + A\beta)$$

$$I_s = \frac{V_i}{R_i} (1 + A\beta)$$

$$\frac{V_i}{I_s} = R_{if} = \frac{R_i}{1+A\beta}$$

### Effective o/p impedance :-


All independent sources are open chkt. Test current  $I_x$  applied on o/p side.

$$R_{of} = \frac{V_x}{I_x} \quad \left| \begin{array}{l} I_f = \beta I_x \\ \text{Applying KCL to i/p node} \\ \Rightarrow I_i = -I_f \Rightarrow I_i = -\beta I_x \end{array} \right.$$


$$I_x = A I_i + \frac{V_x}{R_o} = -A\beta I_x + \frac{V_x}{R_o}$$

$$\frac{V_x}{R_o} = I_x(1+A\beta) \Rightarrow \frac{V_x}{I_x} = R_o(1+A\beta)$$



$$\Rightarrow R_{of} = R_o(1+A\beta)$$

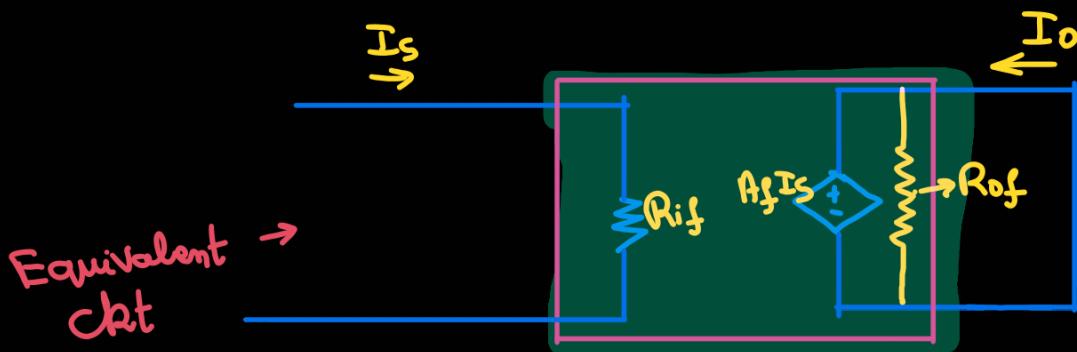

## # Current Series Feedback :-

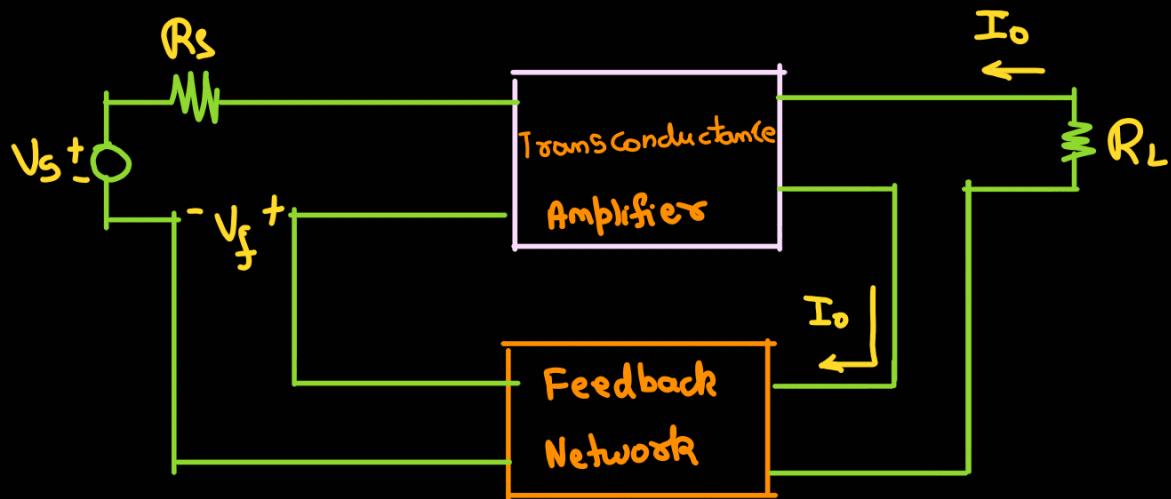

Transconductance Amplifier

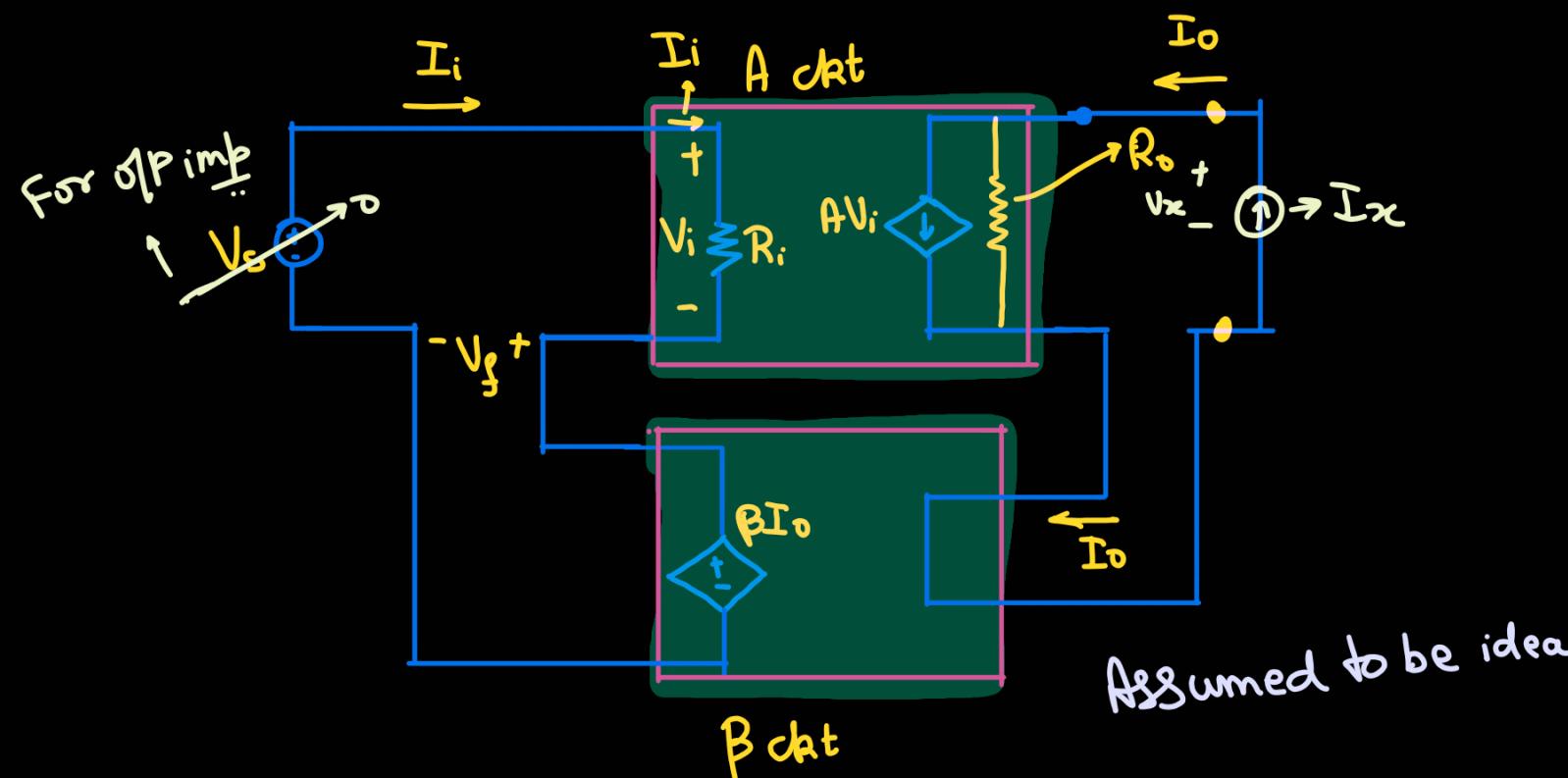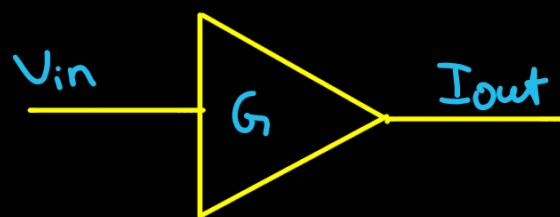

\* Effective I/P &  $\sigma/P$  impedances:-



Use same logic as above 3.

$$R_{if} = R_i [1 + A\beta] \quad | \quad R_{of} = R_o (1 + A\beta)$$

# OSCILLATORS

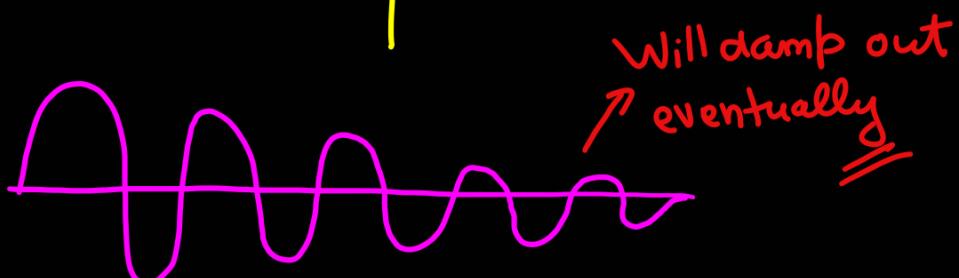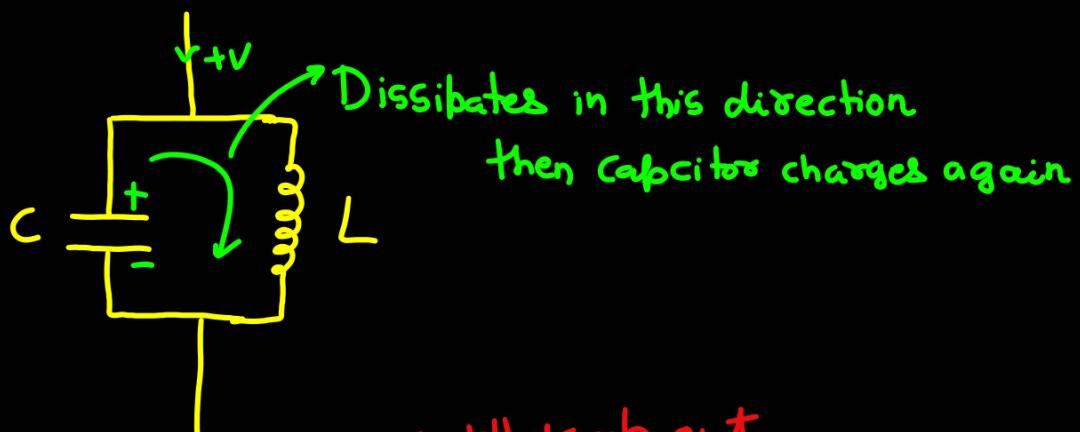
# Tank Circuit:-

An LC parallel ckt is called Tank circuit



$$f = \frac{1}{2\pi\sqrt{LC}}$$

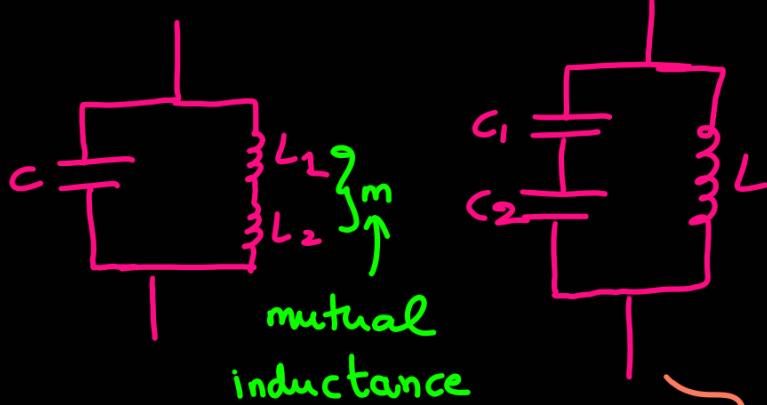This much voltage must be regularly supplied to sustain output.



We can split either C or L in Tank Ckt and get same freq.


$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$L = L_1 + L_2 + 2M$$

Gain =  $A$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$C = \frac{C_1 C_2}{C_1 + C_2}$$

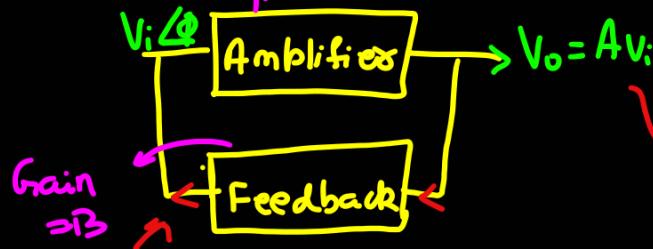

Overall Gain  
 $= Loop Gain = A \times B = 1$   
 Gain  $\leftarrow$  Always 1

Output out of phase by  $180^\circ$

Phase Shift of additional  $180^\circ \Rightarrow \text{Total } \Delta\phi = 360^\circ$

## # Conditions for sustained oscillations:-

These conditions are called Barkhausen's criteria

→ Loop Gain = 1

→ Overall phase shift in the loop must be  $0^\circ/360^\circ$

## # Oscillators:-

An amplifier with +ve feedback network & that can sustain O/P based on Barkhausen's Criteria is called oscillator




## # Types of oscillators:-

- Hartley oscillator
- Colpitts oscillator
- RC phase shift oscillator
- Crystal oscillator

→ These are Radio freq  
or high freq oscillators

→ Audio freq, or low freq, oscillators

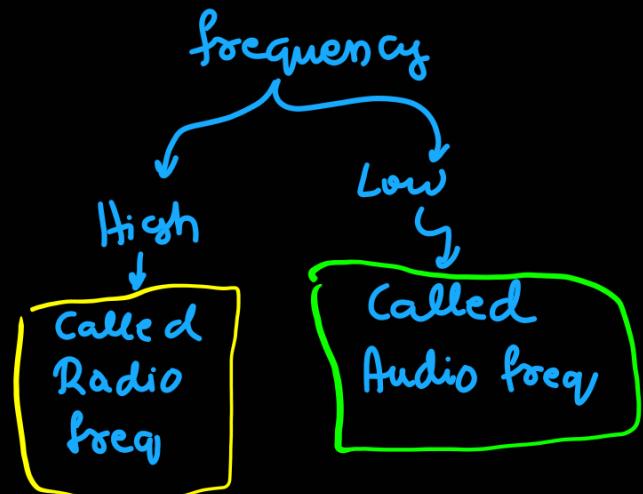


$L \& C$  is not used for low frequency oscillations as the circuit will become lengthy.

Thus only  $R \& C$  are used for AF

## # Hartley oscillator :-

$\hookrightarrow H \rightarrow$  Inductance

$\hookrightarrow$  Split the inductors

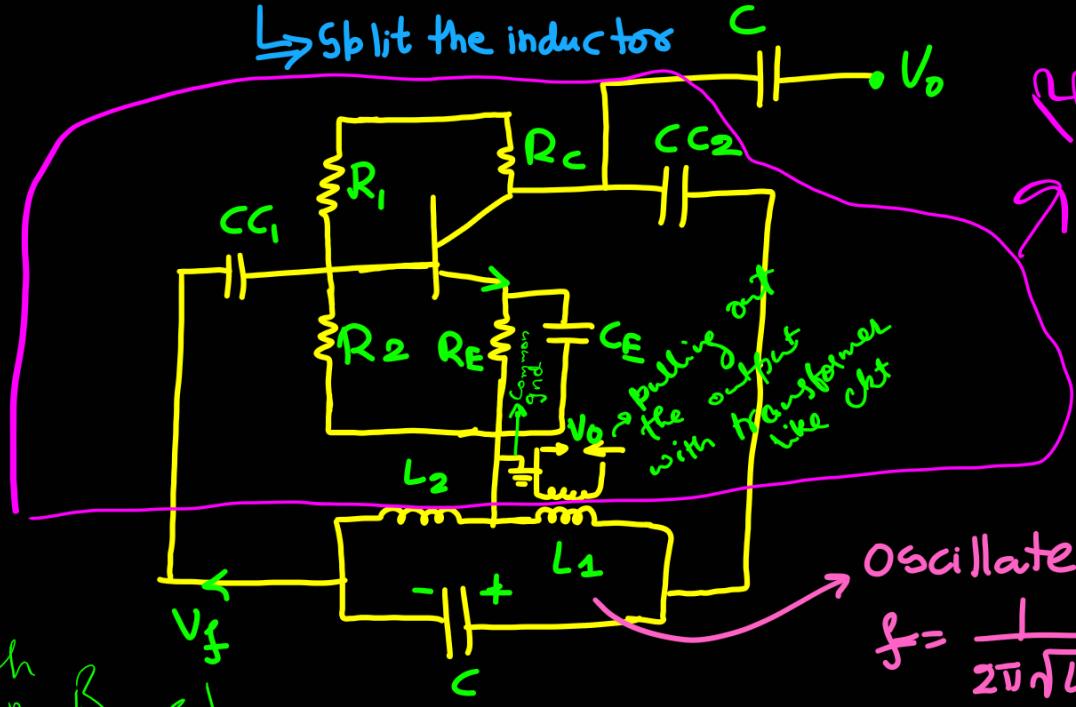

By deficit  
for amplifying

with gain  $\beta$

Explain the det  $\Rightarrow$  Amp, Tank det, then  
output can be taken  
before CC<sub>2</sub> or across L<sub>1</sub>

To prove Barkhausen Criteria:-

$$1) AB = 1$$

$$2) \text{overall phase shift} = 0^\circ / 360^\circ$$

$$V_o = V_i \underline{180^\circ} (A = 1)$$

$$V_f = V_o \underline{180^\circ} (\beta = 1)$$

$$\text{Wkt, } V_i = V_f \underline{\phi} = V_o \underline{180^\circ}$$

$$\text{but } V_o = V_i \underline{180^\circ}$$


$$\therefore V_i = V_f \underline{180^\circ} \underline{180^\circ} \Rightarrow V_i = V_f \underline{360^\circ} \Rightarrow \text{Criteria ①}$$

$$B = \frac{\text{Op voltage}}{\text{Ip voltage}} = \frac{V_f}{V_o} = \frac{X_{L_1}}{X_{L_2}} = \frac{\omega L_1}{\omega L_2} = \frac{L_1}{L_2}$$

$$A = \frac{L_2}{L_1} \Rightarrow A = \frac{1}{B} \Rightarrow AB = 1$$
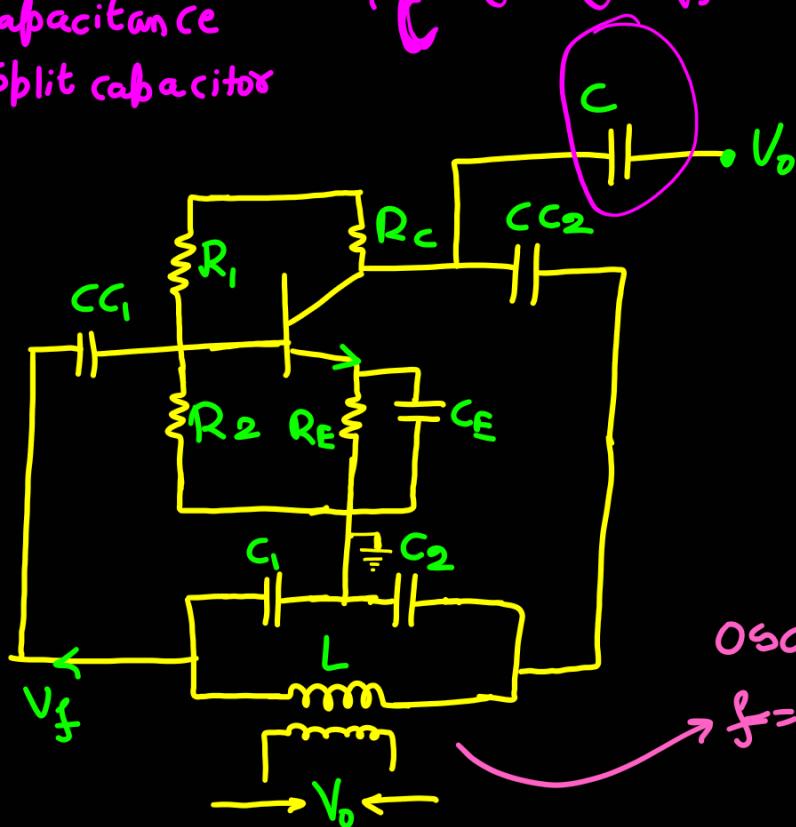
# Colpitts oscillator:-  
 ↳ C → capacitance  
 ↳ Split capacitor

This 'C' for ↓ i.e. reducing noise  
 better output



Oscillate at freq,  
 $f = \frac{1}{2\pi\sqrt{LC}}$   
 where  $C = \frac{C_1 C_2}{C_1 + C_2}$

Explain the det → Amp Tank det, then  
 output can be taken  
 before CC\_2 or across L

To prove Barkhausen Criteria:-

- 1)  $AB = 1$
- 2) overall phase shift =  $0^\circ / 360^\circ$

$$\left. \begin{array}{l} V_f = i X_{C_1} = \frac{i}{\omega C_1} \\ V_o = i X_{C_2} = \frac{i}{\omega C_2} \end{array} \right| \quad B = \frac{V_o}{V_f} = \frac{\frac{i}{\omega C_2}}{\frac{i}{\omega C_1}} = \frac{C_1}{C_2}$$


If  $A = \frac{C_2}{C_1}$  then oscillations will be sustained

Phase diff expl^n same  $\Rightarrow$  Prove Barkhausen Criteria

## #RC phase shift oscillator:-

360° overall shift

Feedback network

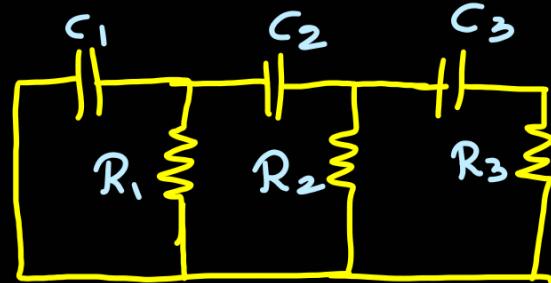

At eq<sup>m</sup> frequency,  
phase shift is 60° in  
each loop.


⇒ Max phase shift = 180°

Eq<sup>m</sup> frequency =  $f = \frac{1}{2\pi RC\sqrt{6}}$

$$R_1 = R_2 = R_3 = R$$

$$C_1 = C_2 = C_3 = C$$

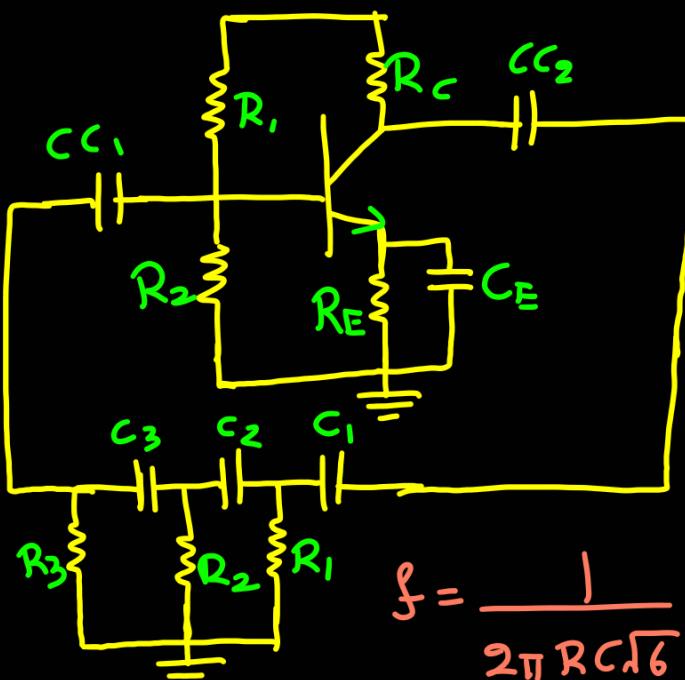for other freq., the phase shift in each loop goes to 90°, so  $90 \times 3 = 270^\circ$



$$f = \frac{1}{2\pi RC\sqrt{6}}$$

At  $f \Rightarrow$  phase shift in each RC network is 60°, ∴ Total feed back network phase shift is 180°

Amplifier  $\beta S = 180^\circ \Rightarrow$  Total = 360° → Barkhausen Criteria 1 satisfied

Barkhausen

Criteria 1 satisfied

The gain of the 3 RC network is  $\perp \Rightarrow B = \frac{1}{29}$

∴ If  $A = 29$ , then  $AB = 1 \Rightarrow$  B.C 2

Satisfied

## # Crystal oscillator:-

Made of quartz  $\rightarrow$  Property  $\rightarrow$  Piezo electric property

Application of pressure creates electrical energy


Application of pressure creates electrical energy


Mechanical energy is converted to electrical energy and vice-versa

We need the crystal to vibrate in order to generate oscillations.


We now apply variable voltage to the crystal to produce vibrations, these vibrations then create oscillatory current!
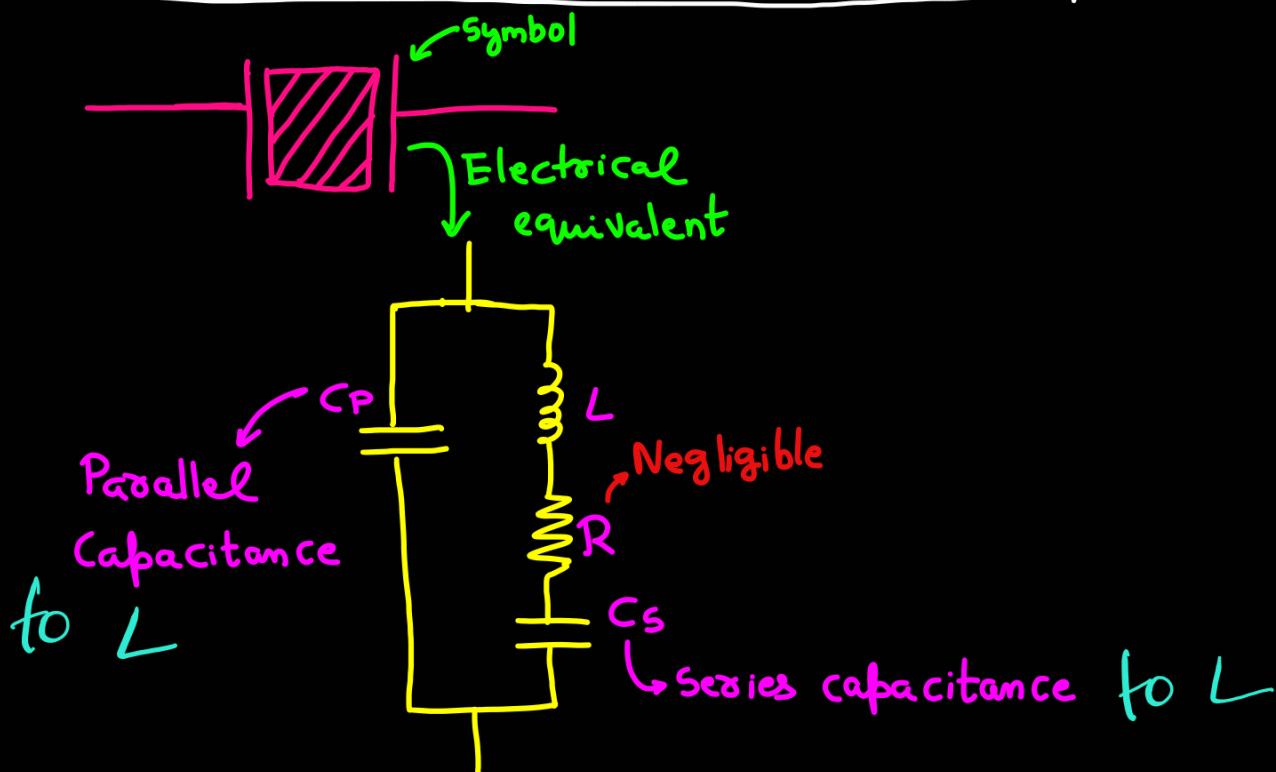
## # Electrical Equivalent ckt of crystal :-



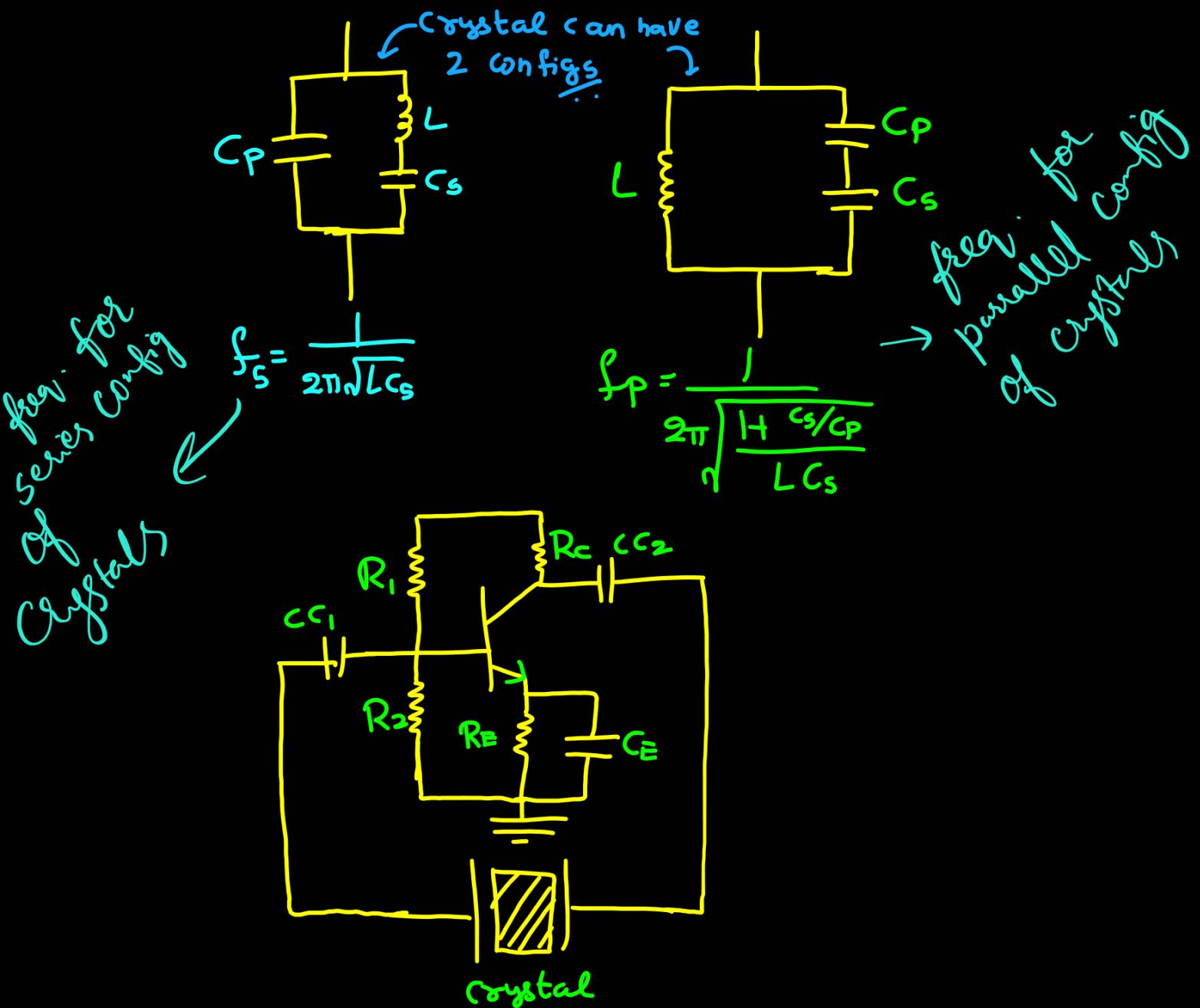
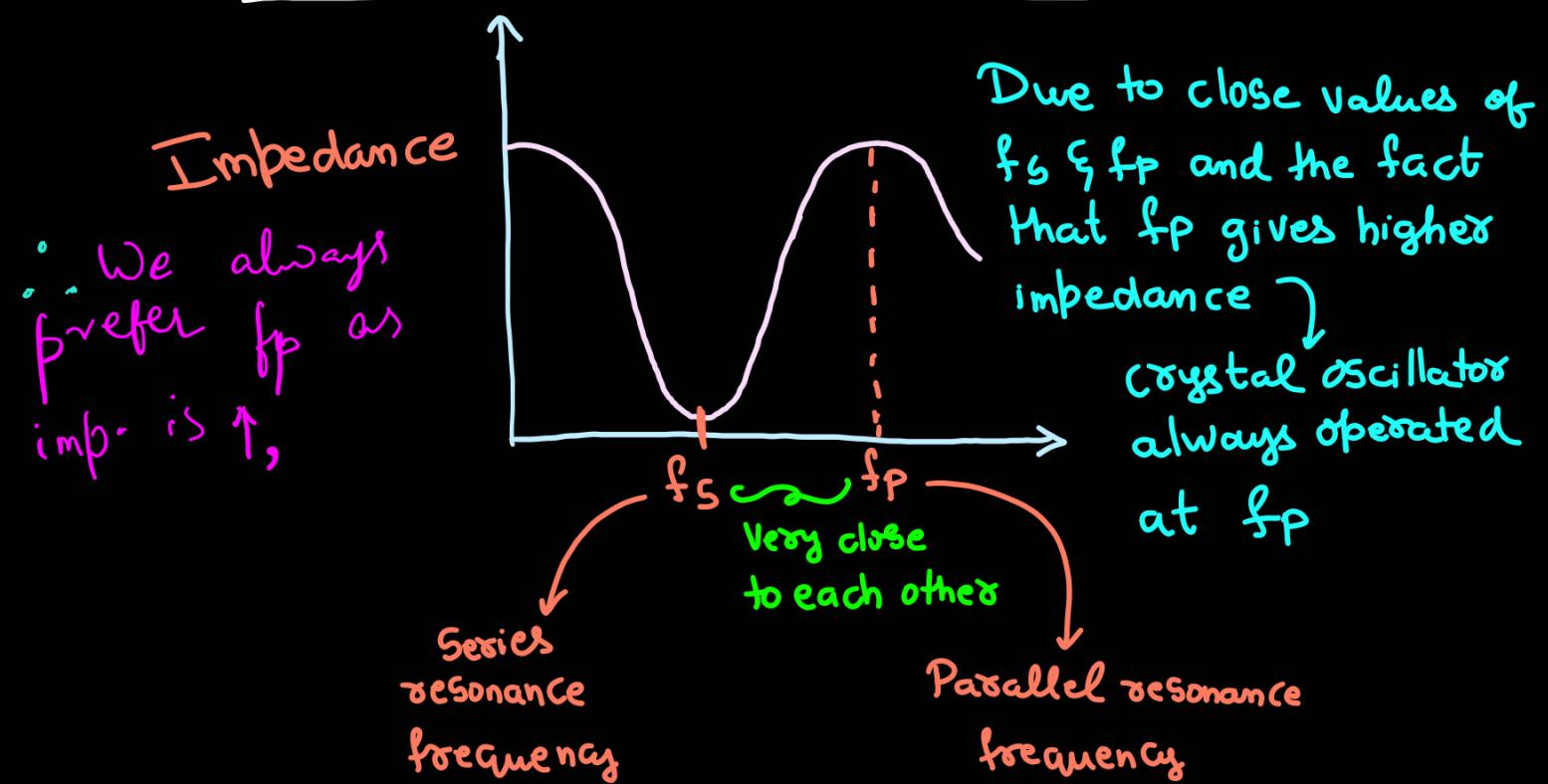
## # Impedance characteristics of crystals:-



\* The material size is almost constant for variable app<sup>n</sup> of temp, thus f is stable

Unlike in LC, in which L & C are likely to change, thus freq, may be unstable & need more economy to stabilise


∴ Crystal oscillator is more stable

### # Additional points:-


\* RC not preferred for high freq oscillators as RC becomes too low.

\* To avoid power dissipation we replace  $R_c$  in amplifier with an inductor called Radio Frequency coil (RFC)

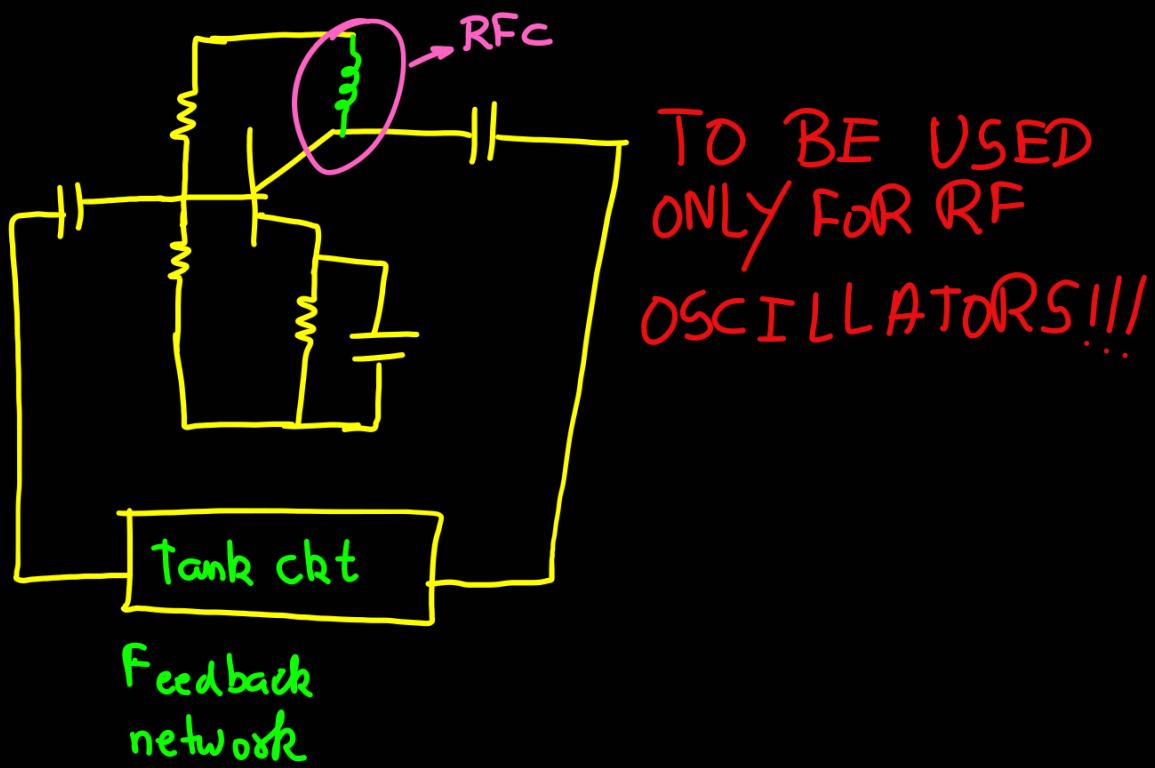
Advantage:- DC power in the collector resistor reduces, thus not draining input very quickly.




## # Wein Bridge Oscillator:-

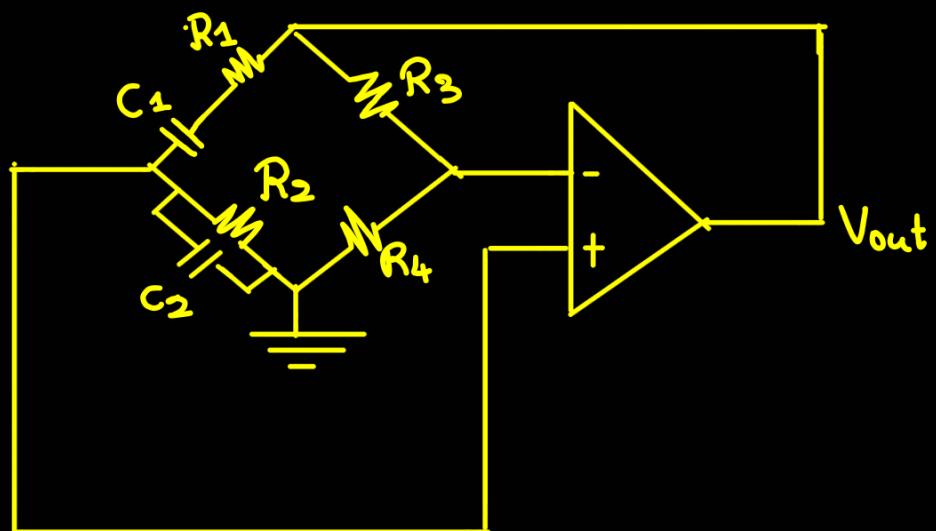

Redrawing this, we get

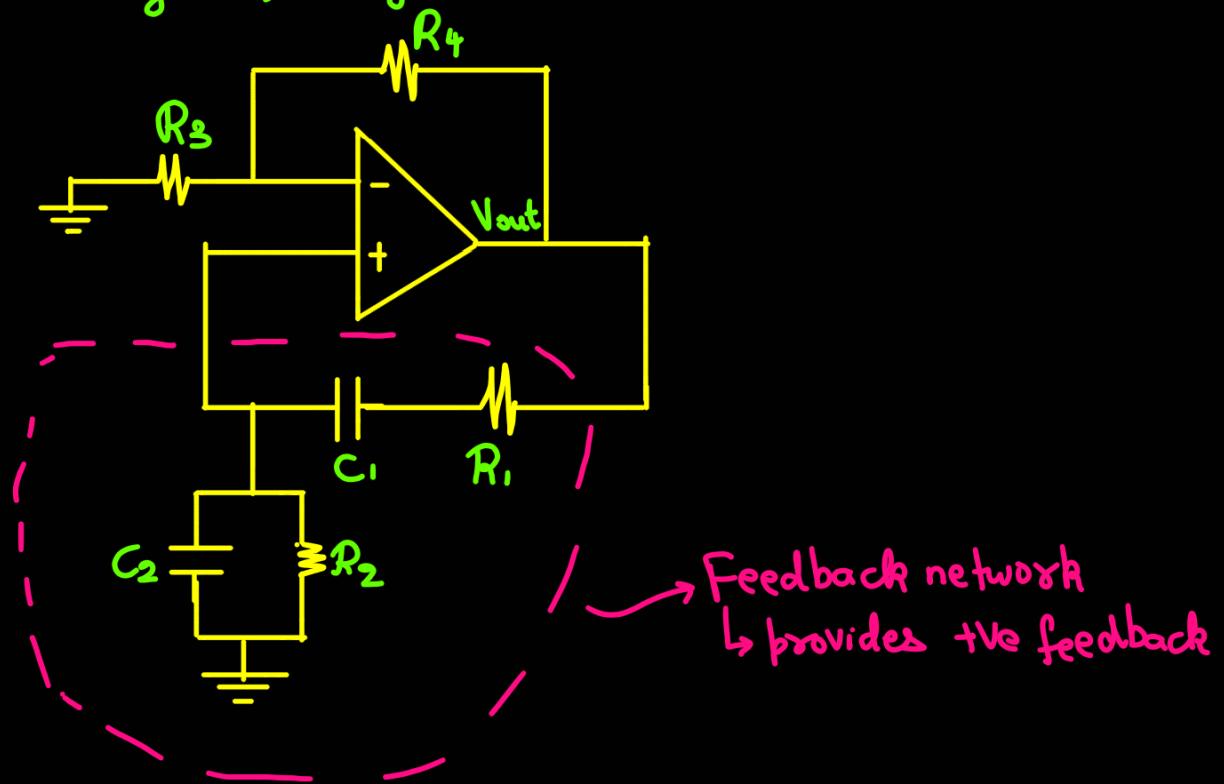

Consider the feedback network:-

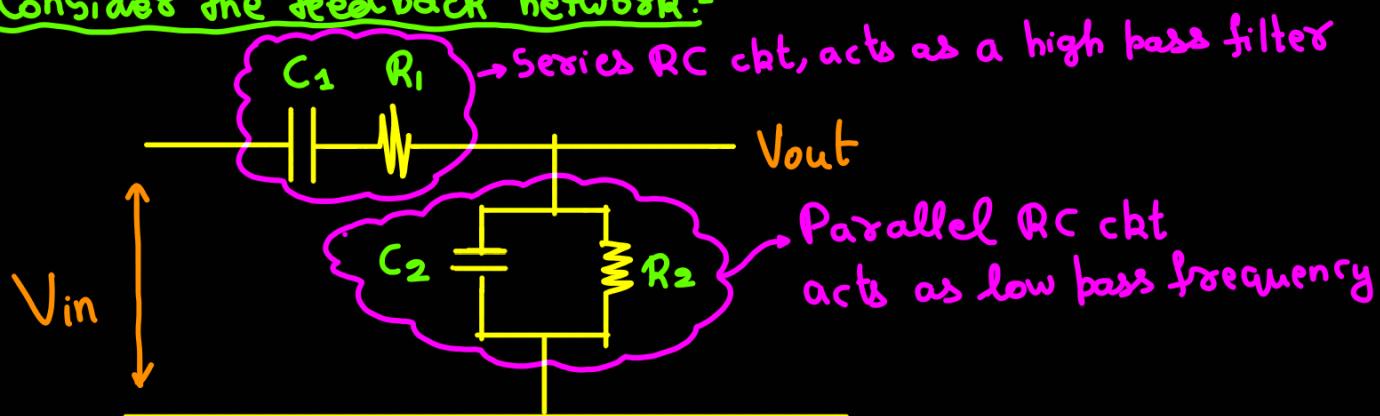

$f_r \rightarrow$  resonant frequency

Response at  $f_r \rightarrow$  

At  $f_r$ , phase shift  $\phi = 0$  &  $\frac{V_o}{V_{in}} = \frac{1}{3}$

If  $R_1 = R_2 \& C_1 = C_2$ , then:-

$$f_r = \frac{1}{2\pi RC}$$